



**2015 Technological Studies**

**Advanced Higher**

**Finalised Marking Instructions**

© Scottish Qualifications Authority 2015

The information in this publication may be reproduced to support SQA qualifications only on a non-commercial basis. If it is to be used for any other purposes written permission must be obtained from SQA's NQ Assessment team.

Where the publication includes materials from sources other than SQA (secondary copyright), this material should only be reproduced for the purposes of examination or assessment. If it needs to be reproduced for any other purpose it is the centre's responsibility to obtain the necessary copyright clearance. SQA's NQ Assessment team may be able to direct you to the secondary sources.

These Marking Instructions have been prepared by Examination Teams for use by SQA Appointed Markers when marking External Course Assessments. This publication must not be reproduced for commercial or trade purposes.

## **Part One: General Marking Principles for: Technological Studies Advanced Higher**

This information is provided to help you understand the general principles you must apply when marking candidate responses to questions in this Paper. These principles must be read in conjunction with the specific Marking Instructions for each question.

- (a) Marks for each candidate response must always be assigned in line with these general marking principles and the specific Marking Instructions for the relevant question. If a specific candidate response does not seem to be covered by either the principles or detailed Marking Instructions, and you are uncertain how to assess it, you must seek guidance from your Team Leader/Principal Assessor.
- (b) Marking should always be positive ie, marks should be awarded for what is correct and not deducted for errors or omissions.


### **GENERAL MARKING ADVICE: Technological Studies Advanced Higher**

The marking schemes are written to assist in determining the “minimal acceptable answer” rather than listing every possible correct and incorrect answer. The following notes are offered to support Markers in making judgements on candidates’ evidence, and apply to marking both end of unit assessments and course assessments.

**Part Two: Marking Instructions for each Question**


**Section A**

**Q1 (a)**

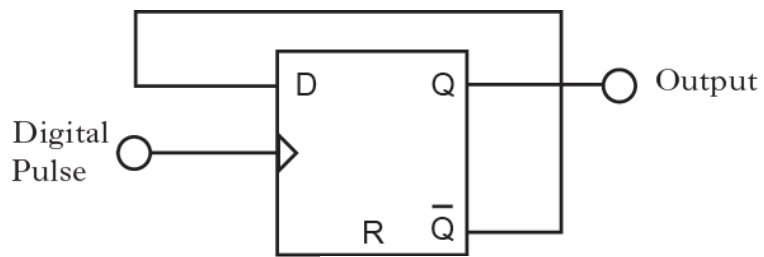


Marks	
2	
6	
2	
<b>(10)</b>	

**(b)**

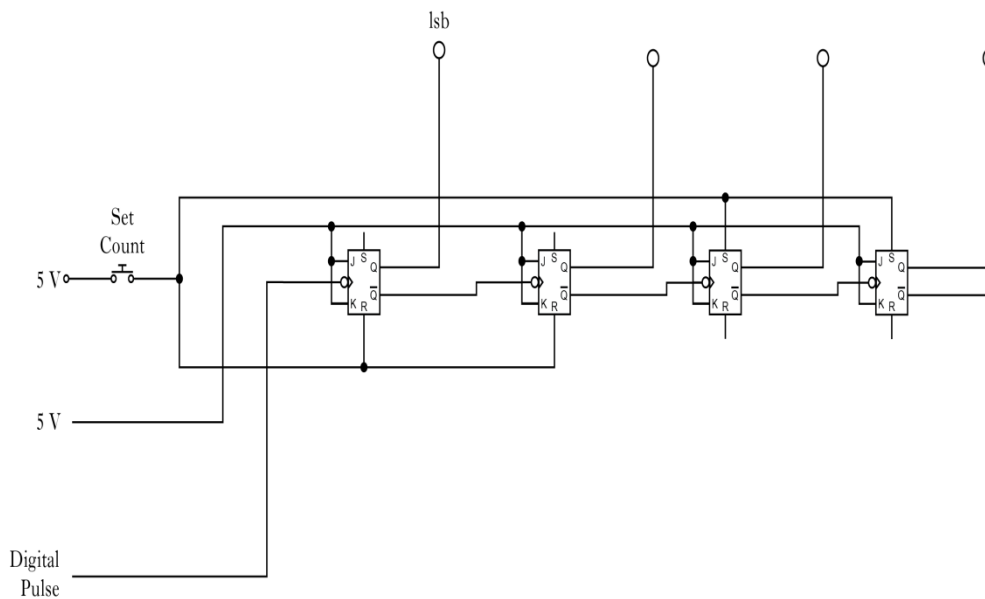


**(c)**  $1024 = 2^{10} = 10$


Q2 (a) (i)

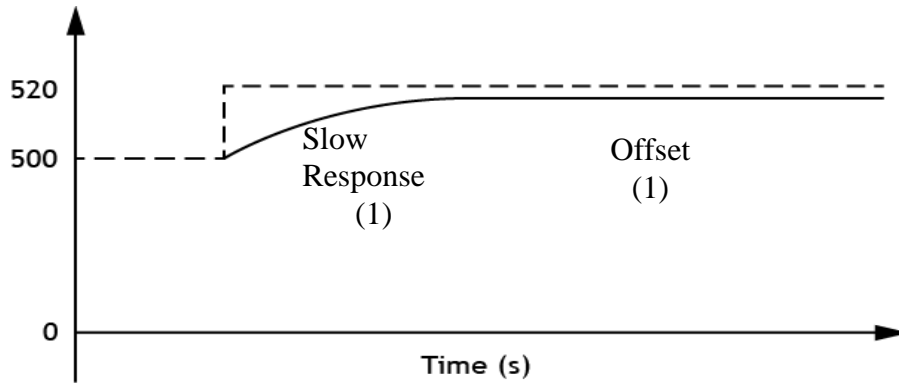

(ii)

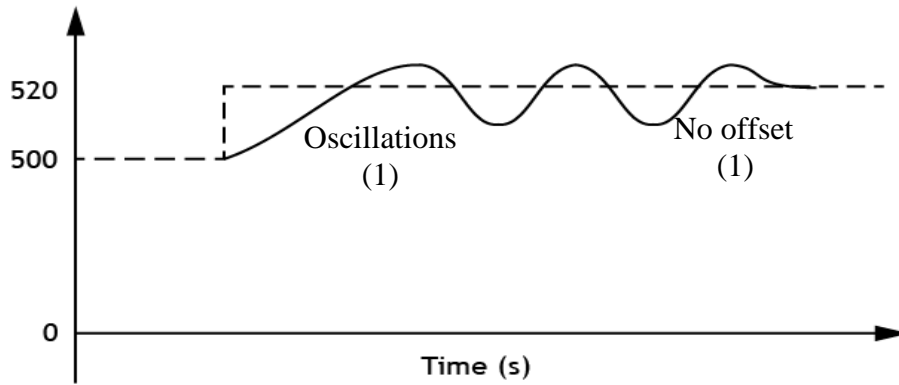

(iii)

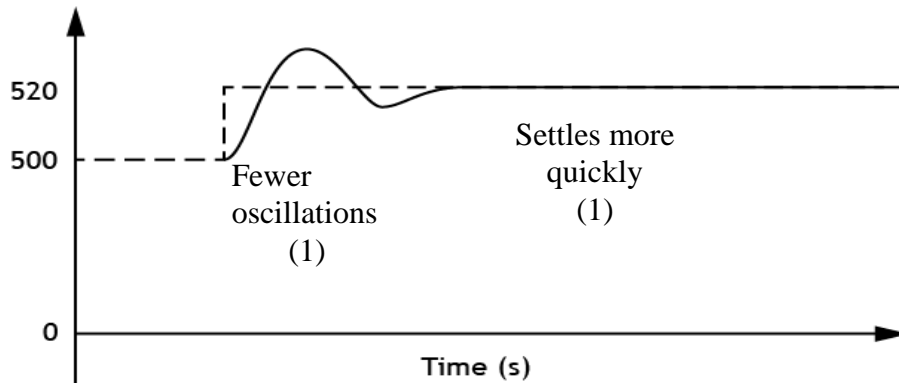

(b) PID control adds extra functions to proportional control in ideal conditions. While proportional tries to minimise the error, PI eliminates it, but PID eliminates it with a faster response time.

Marks	
	2
	2
	2
	3
	(9)

Marks	
1	
1	
3	
1	
1	
2	
1	<b>10</b>
2	
1	<b>3</b>
1	
1	<b>2</b>
	<b>(15)</b>

**Q3 (a)**  $I = bd^3 / 12$   
 $= 100 \times 100^3 / 12$   
 $= 8.33 \times 10^6 \text{ mm}^4$

$y = 50 \text{ mm}$

$M = \sigma I / y$   
 $= 220 \times 8333333.3 / 50$   
 $M = 36.7 \times 10^6 \text{ Nmm}$

$M = \frac{\omega L^2}{8}$

$L = [ 8M / \omega ]^{1/2}$   
 $= [ 8 \times 36,666,666.67 / 7.65 ]^{1/2}$   
 $L = 6.19 \text{ m}$

**(b)**  $M/I = \sigma/y = E/R$   
 $R = ( E y ) / \sigma$   
 $= ( 196000 \times 50 ) / 220$   
 $R = 44.5 \text{ m}$

**(c)** Reduced weight

Increased strength/weight ratio

Any one point per mark.

			<b>Marks</b>	
<b>Q4 (a)</b>	10 digital inputs			
	Analogue input			
	1 ADC			
	LCD output			
	Flash/EEPROM			
	Internal memory			
	4 outputs			
	Internal clock			
		<b>Any six points 1 mark each</b>		<b>6</b>
<b>(b)</b>	Plan the program			
	Write the code	text editor		
	Assemble the code	assembler		
	Download to PIC	programmer		
	Test the program	Download cable		
			<b>Any six</b>	<b>6</b>
				<b>(12)</b>
<b>Q5 (a)</b>	Sub A = RC circuit, charges via 1K & 1M		2	
	Sub B = voltage divider, provides 1/3 & 2/3 reference voltages		2	
	Sub C = two comparators, comparing capacitor voltage with ref voltages		1	
	Sub D = SR bistable, set and reset by comparators		2	
	Sub E = DPDT relay, used to:-		1	
	discharge capacitor when voltage > 2/3,		1	
	charge up capacitor when voltage < 1/3, provide flashing switching for lamp		1 1	
				<b>11</b>
<b>(b)</b>	Limited frequency range due to being a mechanical device.		1	
	Wear of components means it has a finite life		1	<b>2</b>
				<b>(13)</b>

					Marks	
Q6 (a)	main:	bcf	PORTB,3	;mux measure left wheel		
		call	adcread			
		movwf	LEFTSPEED			
		bsf	PORTB,3			
		call	adcread			
		movwf	RIGHTSPEED	;mux measure right wheel		
		movfw	RIGHTSPEED	;subtract		
		subwf	LEFTSPEED,W			
		btsc	STATUS,Z	;zero error		
		goto	main			
		btfs	STATUS,C	;carry bit means + error (or zero)		
		goto	right			
		call	brakeleft			
		goto	main			
		right:	call	brakeright		
	goto	main	1 mark per line			
(b)	brakeleft:	movwf	ERROR			
		rlf	ERROR,F	Double the error value (gain x2)		
		movfw	ERROR	Use as mark value for PWM		
		movwf	MARK		2 marks	
					2	
		comf	MARK,W			
		movwf	SPACE	Use twos complement of mark value as space value		
					2 marks	
					2	
		bsf	PORTB,7			
		movfw	MARK	Apply left brake for MARK ms		
		call	pause			
		bcf	PORTB,7	Release left brake for SPACE ms		
		movfw	SPACE			
		call	pause			
					2 marks	
					2	
	brakeright:	comf	ERROR,F	Do twos complement		
		incf	ERROR,F	Add 1 (correct negative value)		
					2 marks	
					2	
					8	
					(22)	

		Marks	
<b>Q7 (a)</b>	Serial-In-Parallel-Out		<b>1</b>
<b>(b)</b>	Sub A	2-bit binary up counter plus AND gate; Sends pulse to Sub C when count = 3; this enables display	2
	Sub B	3-bit SIPO shift register; Stores a 3-bit binary value	2
	Sub C	binary – 7 seg decoder; converts binary value to decimal; inputs blanked when $\overline{BI}$ low; preventing display of incomplete value	4
	Sub D	7-seg display, displays decimal of number in SIPO; when binary-7seg decoder is enabled	2
			<b>10</b>
			<b>(11)</b>
<b>Q8 (a)</b>	$M = F \times L = 2500 \times 210 = 525000 \text{ Nmm}$ $\sigma = M y / I = [ 525000 \times 25 ] / 260\,000$ $= 50.5 \text{ N/mm}^2$	2 3 1	<b>6</b>
<b>(b)</b>	E for aluminium alloy = $70 \times 10^3 \text{ N/mm}^2$  $\delta = FL^3 / 3EI$ $= 2500 \times 210^3 / 3 \times 70 \times 10^3 \times 260\,000$ $= 2.31525 \times 10^{10} / 5.46 \times 10^{10}$ $= 0.424 \text{ mm}$	1 2 1	<b>4</b>
			<b>(10)</b>



**Q9 (a)**  $V_a = -1 / (1 \times 10^6 \times 1 \times 10^{-6}) \times \int 6 dt$   
 $= -6t$

4


**(b)**  $V_{out} = -1 / (1 \times 10^6 \times 1 \times 10^{-6}) \times \int 6 dt$   
 $= + 6/2 t^2$   
 $= 3 t^2$

4

**(c)**

Time	$V_a$	$V_{out}$
0.0	0	0.00
0.5	-3	0.75
1.0	-6	3.00
1.5	-9	6.75
2.0	-12	12.00
2.5	-12	15.00
3.0	-12	18.00
3.5	-12	18.00
4.0	-12	18.00

5

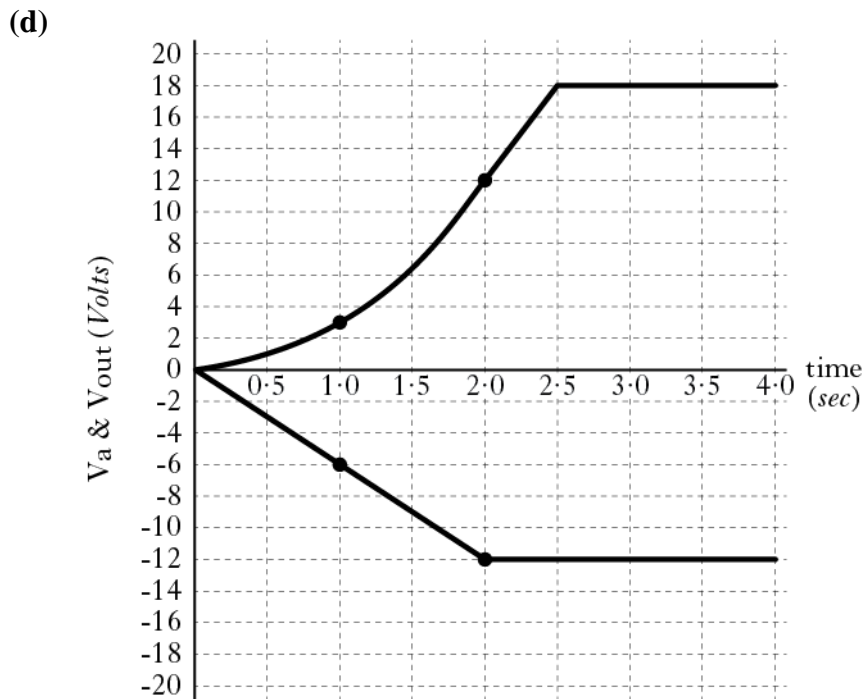

2

3

(18)

Marks	
1	<b>6</b>
1	
1	
1	
1	
1	
1	<b>5</b>
1	
1	
1	
1	
	<b>3</b>
	<b>4</b>

**Q10 (a)** When any LDR goes dark V across it increases  
 Causes Schmitt inverting input to go higher  
 When V- reaches 3V Schmitt saturates low  
 Triggers 555 in monostable mode  
 Pin3 goes high for a time then low  
 This clocks the 3-bit counter

**(b)**  $\frac{R_p}{7} = \frac{2}{3}$

$R_p = 4.67k\Omega$


$10R/(10 + R) = 4.67$

$10R = 46.7 + 4.67R$

$R = 46.7/5.33$

$R = 8.76k\Omega$

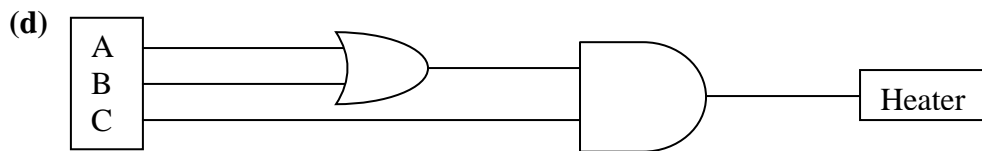**(c)**  $H = (A.\bar{B}.C) + (\bar{A}.B.C) + (A.B.C)$   
 $H = C.(A + B)$




**Q10 (e)** pack:

	btfscl	PORTB,2		1
	goto	weight		1
	btfscl	PORTB,1		1
	goto	plastic		1
	goto	pack		1
weight:	movlw	d'10'		1
	movwf	COUNT		1
loop:	→ bsf	PORTB,7	}	1
	movlw	d '25'		1
	call	pause		1
	→ bcf	PORTB,7	}	
	movlw	d '25'		1
	call	pause		1
	decfsz	COUNT		1
	goto	loop		1
	→ return		both "return"	1
plastic:	movlw	d '6'		1
	movwf	COUNT		1
loop2:	→ bsf	PORTB,6	}	1
	movfw	MARK		1
	call	pause		1
	→ bcf	PORTB,6	}	
	movfw	SPACE		1
	call	pause		1
	rrf	MARK,F		1
	rlf	SPACE,F		1
	decfsz	COUNT,F		1
	goto	loop2		1
	→ return			

**22**

**(40)**

Q11 (a)

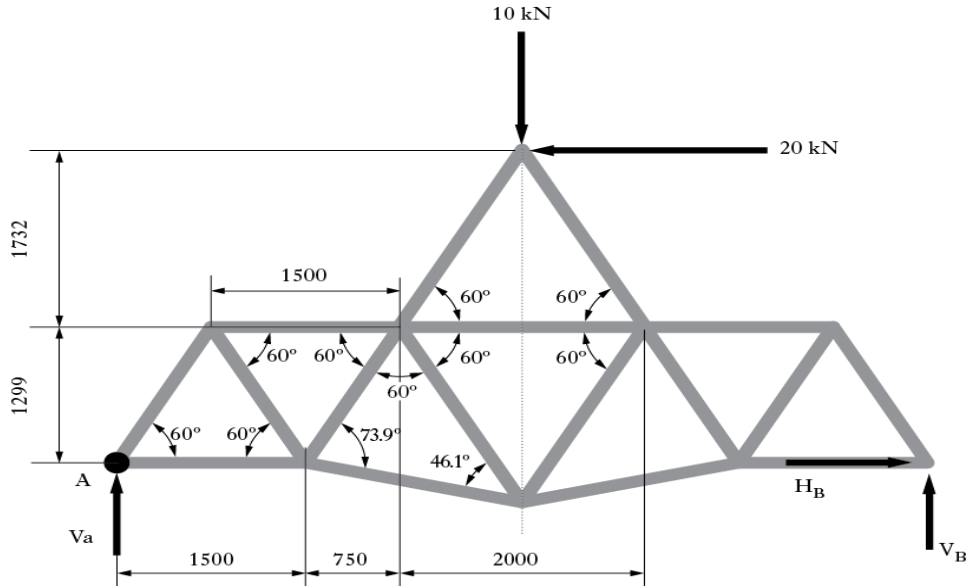

$$\begin{aligned} \underline{\Sigma M_a = 0 \text{ CW}+} \quad & + (10 \times 3250) - (20 \times 3031) - (V_B \times 6500) = 0 \\ & + 32500 \quad - \quad 60620 \quad = + 6500V_B \end{aligned}$$


$$V_B = -28120 / 6500 = -4.33 \text{ kN} \downarrow$$

$$\underline{\Sigma H = 0} \quad H_B = 20 \text{ kN} \rightarrow$$

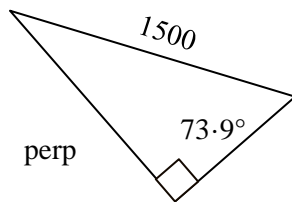(b)  $\underline{\Sigma M_q = 0 \text{ CW}+}$   $-(F_1 \times 1299) + (4.33 \times 1500) = 0$   
 $-1299F_1 + 6495 = 0$   
 $F_1 = + 5 \text{ kN (tie)}$

$$\begin{aligned} \underline{\Sigma M_p = 0 \text{ CW}+} \quad & + (4.33 \times 2250) - (20 \times 1299) + (F_3 \times 1441) = 0 \\ & + 9742.5 \quad - 25980 \quad + 1441F_3 = 0 \\ F_3 = + 11.27 \text{ kN TIE} \end{aligned}$$

$$\begin{aligned} \underline{\Sigma V = 0 \uparrow+} \quad & -11.27 \sin 13.9^\circ - 4.33 + F_2 \sin 60^\circ = 0 \\ & -2.71 \quad - 4.33 + 0.866F_2 = 0 \\ F_2 = + 8.13 \text{ kN (TIE)} \end{aligned}$$



$$\begin{aligned} \sin 73.9^\circ &= \text{perp} / 1500 \\ \text{perp} &= 1500 \times \sin 73.9^\circ \\ &= 1441 \text{ mm} \end{aligned}$$

3  
1  
2  
1


7

2  
1  
2  
3  
1  
2

17

Marks	
2	
1	
1	
1	
1	
2	
8	
8	
(40)	

Q11 (c)

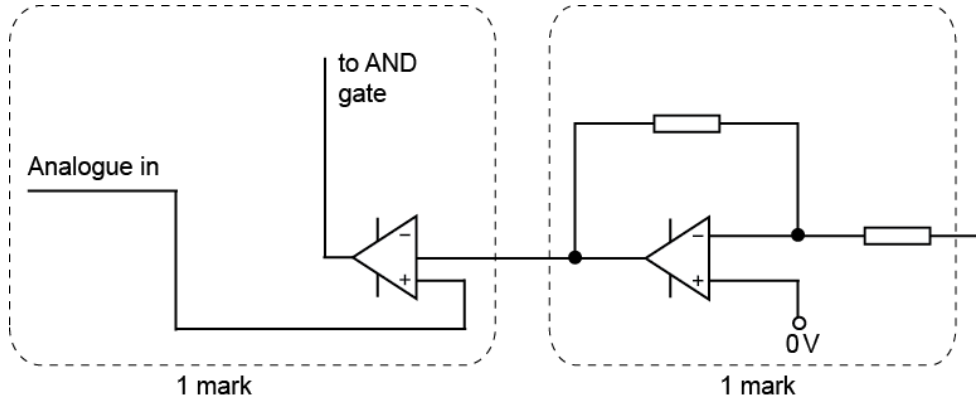

$2.555/511 = 0.005$  resolution


$(2 / R_0) \times 5 = 0.005$

$R_0 = (2 \times 5) / 0.005$

$R_0 = 2000 \text{ k}\Omega$

- $R_0 = 2000 \text{ k}\Omega$
- $R_1 = 1000 \text{ k}\Omega$
- $R_2 = 500 \text{ k}\Omega$
- $R_3 = 250 \text{ k}\Omega$
- $R_4 = 125 \text{ k}\Omega$
- $R_5 = 62.5 \text{ k}\Omega$
- $R_6 = 31.3 \text{ k}\Omega$
- $R_7 = 15.6 \text{ k}\Omega$
- $R_8 = 7.8 \text{ k}\Omega$

Q11 (d)

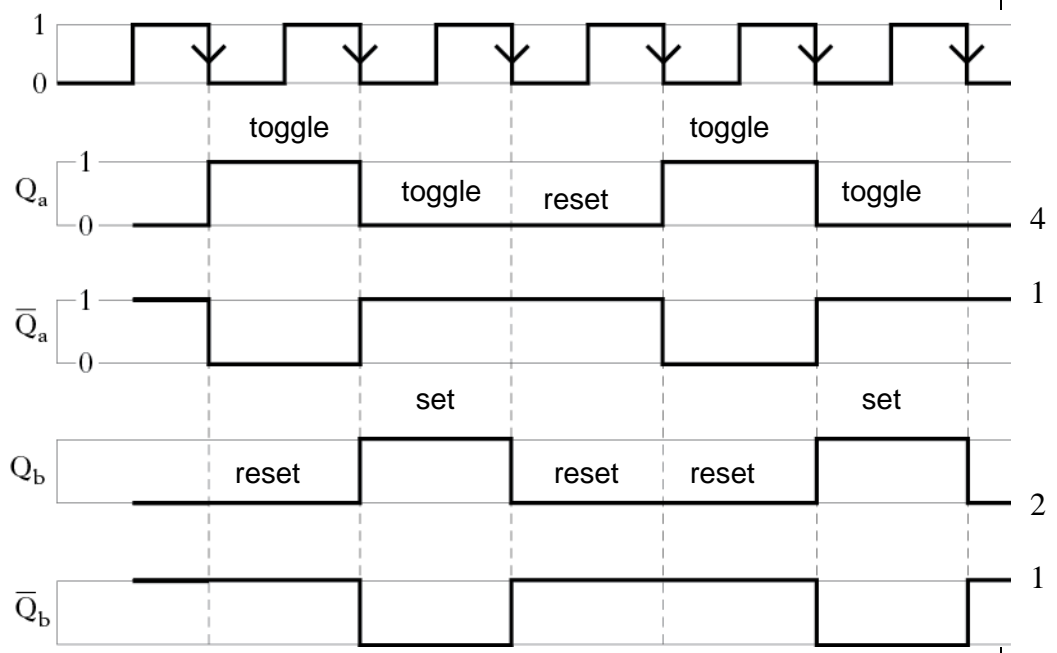

			Marks			
Q12 (a)	main:	movlw	d '25'	}	1	
		movwf	LOOPCOUNT			
	loop:	btfsc	PORTB,0	}	1	
		incf	PULSECOUNT,F			
		movlw	d '1'	}	1	
		call	pause			
		decfsz	LOOPCOUNT	1		
		goto	loop	1		
		movlw	d '10'	}	1	
		subwf	PULSECOUNT,W			
		btfss	STATUS,C	1		
		goto	bleep	1		
		movfw	PULSECOUNT	1		
		sublw	d '13'	}	1	
		btfss	STATUS,C			
		goto	bleep	1		
		bsf	PORTB,7	}	1	
		movlw	d '80'			
		call	pause	}	1	
		bcf	PORTB,7			
		bleep:	bsf	PORTB,6	}	1
			movlw	d '150'		
			call	pause	}	1
		bcf	PORTB,6			
		movfw	PULSECOUNT	}	1	
		sublw	d '23'			
		btfsc	STATUS,C	1		
		goto	main	1		
		bsf	PORTB,5	}	1	
		movlw	d '2'			
		call	pause	}	1	
		bcf	PORTB,5			
		goto	main		21	
(b)	$I_{\text{solid}} = BD^3/12$				1	
	$= 11 \times 20^3/12 = 7333$					
	$I_{\text{hole}} = 9 \times 16^3/12 = 3072$				1	
	$I_{xx} = 4261 \text{ mm}^4$				1	
					<b>3</b>	


**Marks**

**Q12 (c)**  $\Sigma M = 0$  about  $R_2$ :

$$+(R_1 \times 250) - \left( 25 \times 250 \times \frac{250}{2} \right) - (1200 \times 70) = 0$$

$$R_1 = 3.46 \text{ kN}$$

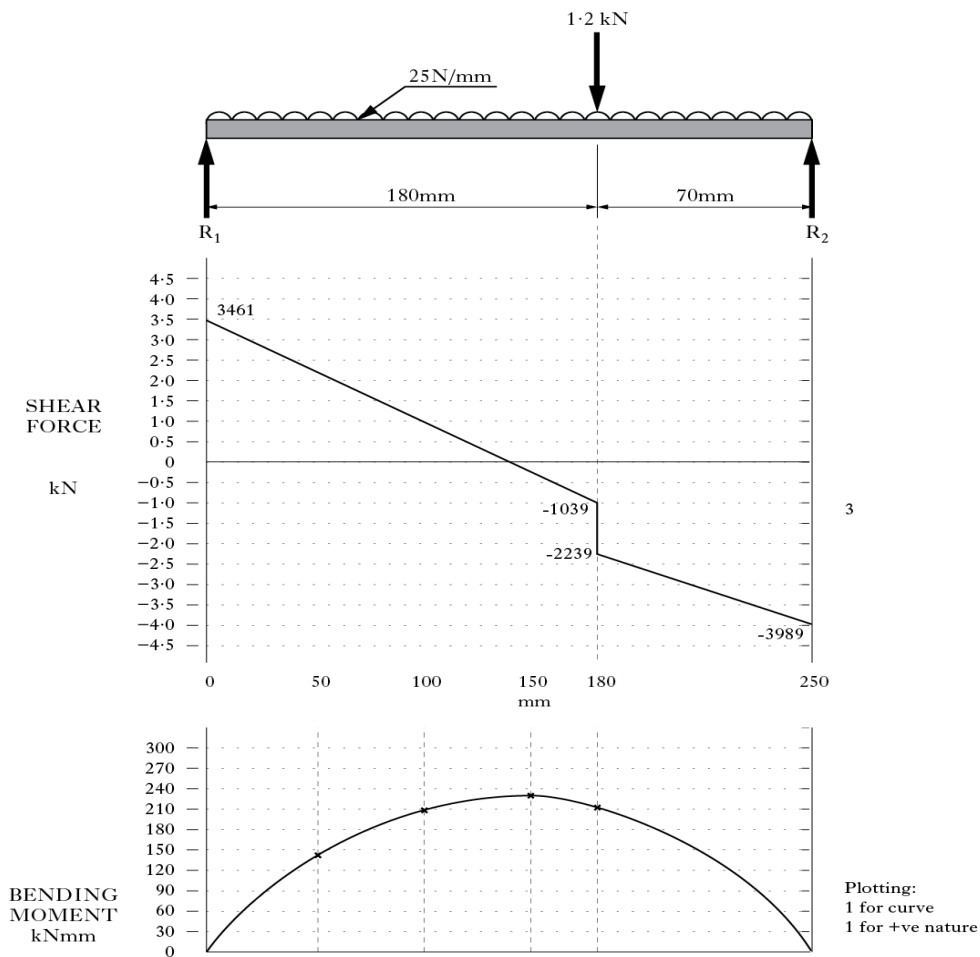- (d) 50:  $3461 \times 50 - 25 \times 50^2 / 2 = 141800 \text{ Nmm} = 142 \text{ kNmm}$   
 100:  $3461 \times 100 - 25 \times 100^2 / 2 = 221100 \text{ Nmm} = 221 \text{ kNmm}$   
 150:  $3461 \times 150 - 25 \times 150^2 / 2 = 237900 \text{ Nmm} = 238 \text{ kNmm}$   
 180:  $3461 \times 180 - 25 \times 180^2 / 2 = 217980 \text{ Nmm} = 218 \text{ kNmm}$



Distance from LHE (mm)	0	50	100	150	180	250
Bending Moment (kNmm)	0	142	221	238	218	0

1      2      2      2      2

1

1      2

3

2

9

**14**  
**(40)**

[END OF MARKING INSTRUCTIONS]